


單選題 (10 pts, 2 pts each) ※ 注意：請於試卷上「選擇題作答區」依序作答。

1. Choose the power amplifier configuration that has the lowest power dissipation during quiescent situation (i.e., no signal input), and the highest power conversion efficiency at maximum output amplitude: (A) Class A; (B) Class B; (C) Class AB; (D) They cannot achieve both advantages.
2. Which of the following is not a function of Miller frequency compensation? (A) Bandwidth extension of the forward amplifier; (B) Feedback stability when used with external resistive feedback; (C) Efficient compensation without using large capacitor values; (D) To move the frequency location of the original dominant pole.
3. Choose the single configuration that is best suitable for implementation of CMOS static memory address decoder: (A) Pseudo NMOS NOR logic; (B) Pseudo-NMOS NAND logic; (C) CMOS NOR logic; (D) CMOS NAND logic.
4. Choose the single correct statement about common-drain-common-source cascade amplifier: (A) The common-drain stage increases the input impedance; (B) The common-source stage provides low output impedance; (C) The use of the common-drain stage provides a low-impedance node to widen the frequency bandwidth; (D) The use of common-source stage provides a current buffer to increase the open-circuit output voltage gain.
5. Choose the single incorrect statement about folded-cascode differential amplifier, as compared with cascode differential amplifier: (A) It achieves the purpose of level shifting; (B) It achieves the purpose of increased input common-mode range; (C) It is often better suited for low-voltage applications; (D) It is often much better in terms of frequency response.


接背面

※ 注意：請於試卷上「非選擇題作答區」依序作答，並應註明作答之大題及小題題號。
計算與問答題 (90 pts)

 1. (30 pts) See figure on next page. Neglect all other capacitance and assume $\lambda = 0$.
 - (a) (10pts) Determine the zero of the transfer function without calculating the transfer function.
 - (b) (10 pts) Determine the impedance of the load consisting C_1 , R_1 , and M_2 . (7 pts)
Under what condition does the impedance become inductive? (3 pts)
 - (c) (10 pts) Determine the overall transfer function of the amplifier.




 2. (30 pts) Given below is a cascode MOS current mirror circuit.
 - (a) (5 pts) Symbolically derive the resistance as seen from the output node. Neglect body effect for simplicity.
 - (b) (10 pts) With $V_{SS} = -5$ V, $I_{REF} = 10$ μ A, $V_t = 1$ V, $\mu_n C_{ox} = 20$ μ A/V², $L = 10$ μ m, $W = 40$ μ m, and $V_A = 20$ V. Find the output resistance and the lowest allowable output voltage. Assume all devices are equal.
 - (c) (10 pts) Repeat the above for an NMOS current mirror without using cascode.
 - (d) (5 pts) Explain the benefit of cascode current mirror and its trade-off.




接次頁

3. (21 pts) Consider the following pass-transistor logic circuit. The body effect and subthreshold current are neglected in this problem. Note that $V_{tn} = 0.7$ V and $|V_{tp}| = 0.6$ V.
- (a) (2 pts) $V_A = 3$ V, $V_B = 3$ V, what is the steady-state voltage for V_X ?
- (b) (5 pts) Repeat part (a) for $(V_A = 3.5$ V, $V_B = 3$ V) and $(V_A = 4$ V, $V_B = 4$ V)?
- (c) (3 pts) A CMOS inverter (M_{ni} and M_{pi}) is added to obtain full swing at the output of V_Y . What's the maximum V_{dd} to avoid the DC leakage for the input in (a)?
- (d) (5 pts) Use V_{dd} in (c) to design PMOS and NMOS ratio for the CMOS inverter to obtain $V_M = \frac{V_{dd}}{4}$, where V_M is defined as $V_{in} = V_{out} = V_M$.
- (e) (6 pts) Can we express V_Y by $Y = \overline{AB}$? If not, please add NMOS-only transistors to generate NAND function?

 

 4. (9 pts) A single amplifier biquad filter can be implemented as the following circuit. The open-loop gain of the amplifier is A_0 but not infinite.
- (a) (2 pts) What type of filter is it? low pass or ?
- (b) (7 pts) Derive the transfer function and obtain Q and ω_0 .



試題隨卷繳回