

1. Fig.1 shows the schematic of an instrumentation amplifier with $R_2 = R_3 = R_4 = 100 \text{ k}\Omega$, and $2R_1 = 10 \text{ k}\Omega$. All Ops are ideal. Please answer the following questions.
- difference-mode gain; (12 pts)
 - common-mode gain; (12 pts)
 - CMRR. (10 pts)

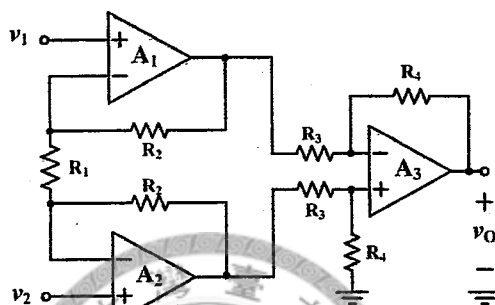


Fig.1

2. Assume all the transistors in Fig.2 have the same characteristics. If $\beta = 200$, $V_A = 100\text{V}$, $T = 290\text{K}$, $V_{CC} = 5\text{V}$, $R_1 = 10 \text{ k}\Omega$ and $R_2 = 11 \text{ k}\Omega$, please solve the following questions. (Note: no points will be given if the problem-solving procedures are not shown)
- common-mode voltage gain (A_{cm}); (5 pts)
 - differential voltage gain (A_d); (5 pts)
 - CMRR; (3 pts)
 - Differential input resistance (R_{id}). (5 pts)

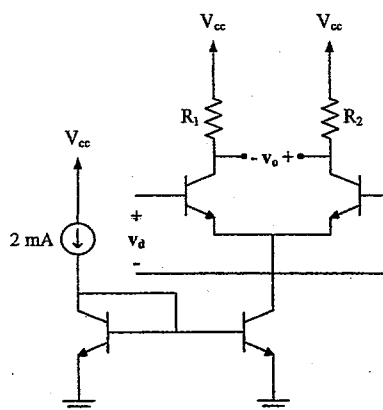


Fig.2

接背面

3. Assume that the two transistors (Q_1 and Q_2) in Fig.3 are operating in the saturation region with different g_m (g_{m1} , g_{m2}) and r_o (r_{o1} , r_{o2}). Please find the following circuit characteristics. The body effect can be neglected for simplicity but the transistor output resistance (r_o) needs to be included in the analysis.
- Input resistance (R_{in}); (5 pts)
 - Output resistance (R_{out}); (5 pts)
 - Small-signal open-circuit voltage gain (v_o/v_{in}). (5pts)

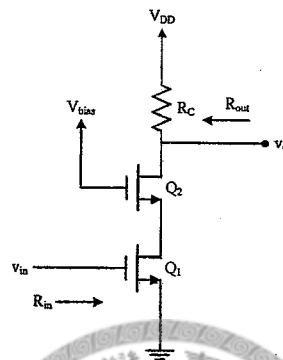


Fig.3

4. For the circuit below (see Fig.4), OP_1 is an ideal opamp, V_1 and V_2 are ideal DC voltage sources, all PMOS transistors have the same size of $(W/L)_p$, and all NMOS transistors are the same with size of $(W/L)_n$. Assume the drain voltages of transistors P_5 and N_3 are biased properly. The threshold voltages of PMOS and NMOS are V_{tp} and V_{tn} , respectively. Assume $(W/L)_p = 2(W/L)_n = (W/L)$, $|V_{tp}| = V_{tn} = V_t$, and $k_n' = 2k_p' = k$ ($k_n' = \mu_n C_{ox}$ and $k_p' = \mu_p C_{ox}$). Ignore the channel-length modulation and body effect.
- If $R_a = R_b = 0$, derive an equation for the drain current (I_1) of transistor N_1 in terms of the circuit and device parameters. (4 pts)
 - Continue from (1), if $V_1 = 4V$, $V_2 = 1V$, $R_1 = 3k\Omega$, $(W/L) = 200$, $V_t = 0.5V$, $k = 100\mu A/V^2$, calculate the value of I_1 . (2 pts)
 - If the circuit output operates like a class-AB stage, explain the purpose and operation of transistors N_2 , P_2 , and resistors R_a , R_b . (3 pts)
 - If $R_a = R_b = R = 200\Omega$, and the other parameters are the same as in (2), calculate the maximum current flowing through the transistor P_1 . (4 pts)

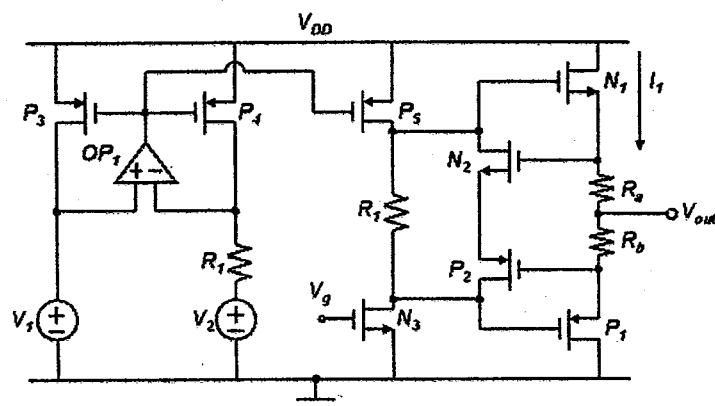


Fig. 4

接
次
頁

試題隨卷繳回